

7

Bipolar Junction Transistor (BJT)

- A three-terminal device that uses the voltage of the two terminals to control the current flowing in the third terminal.
 - The basis for amplifier design.
 - The basis for switch design.
 - The basic element of high speed integrated digital and analog circuits.
- Applications
 - Discrete-circuit design.
 - Analog circuits.
 - * High frequency application such as radio frequency analog circuit.
 - Digital circuits.
 - * High speed digital circuit such as emitter coupled circuit (ECC).
 - * Bi-CMOS (Bipolar+CMOS) circuits that combines the advantages of MOS-FET and bipolar transistors.
 - MOSFET: high-input impedance and low-power.
 - Bipolar transistors: high-frequency-operation and high-current-driving capabilities.
- Circuit symbol
 - The arrowhead on the emitter implies the polarity of the emitter-base voltage.
 - * NPN: $v_{BE} > 0$.
 - * PNP: $v_{EB} > 0$.

7.1 Structure

7.1.1 NPN Transistor

- Figure 7.2 depicts a simplified NPN transistor.
 - Emitter (E): heavily doped n-type region.
 - Base (B): lightly doped p-type region.
 - Collector (C): heavily doped n-type region.
 - Two diodes connected in series with opposite directions.
 - * EBJ: Emitter-Base junction.

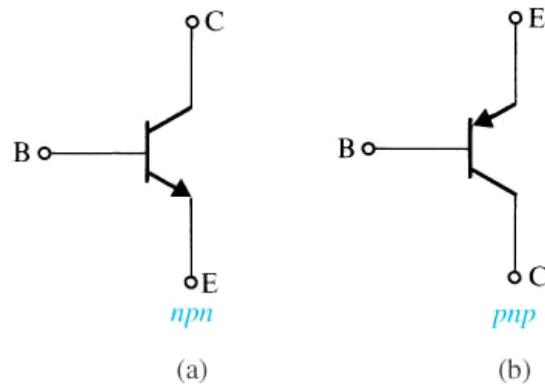


Figure 7.1: Circuit symbols of (a) NPN and (b) PNP transistors.

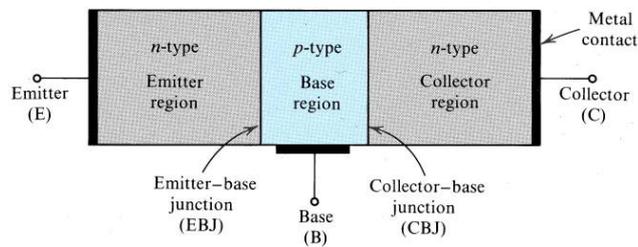


Figure 7.2: A simplified structure of the NPN transistor.

- * CBJ: Collector-Base junction.
- Figure 7.3 shows the cross-section view of an NPN transistor.
 - The NPN transistor has asymmetrical structure.
 - α and β parameters are different for forward active and reverse active modes.
- Modes of operations
 - Cutoff
 - * EBJ (Reverse), CBJ (Reverse)
 - * $v_{BE} < 0, v_{CB} > 0$.
 - Active (refer to Figure 7.7)
 - * EBJ (Forward), CBJ (Reverse)
 - * $v_{BE} > 0, v_{CB} > 0$.
 - Reverse Active
 - * EBJ (Reverse), CBJ (Forward)
 - * $v_{BE} < 0, v_{CB} < 0$.
 - Saturation
 - * EBJ (Forward), CBJ (Forward)
 - * $v_{BE} < 0, v_{CB} < 0$.

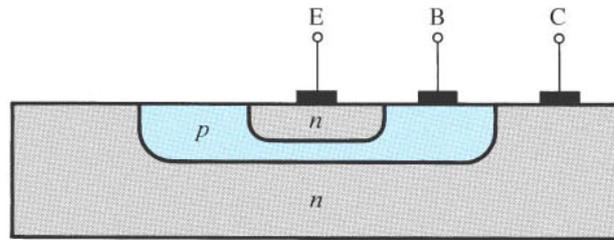


Figure 7.3: Cross-section of an NPN BJT.

- Figure 7.4 shows the voltage polarities and current flow in the NPN transistor biased in the active mode.

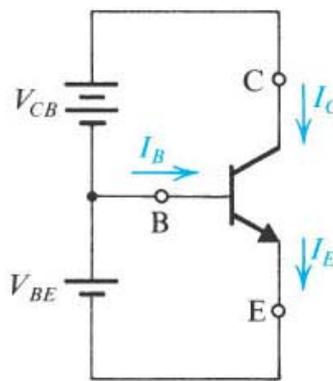


Figure 7.4: Voltage polarities and current flow in the NPN transistor biased in the active mode.

7.1.2 PNP Transistor

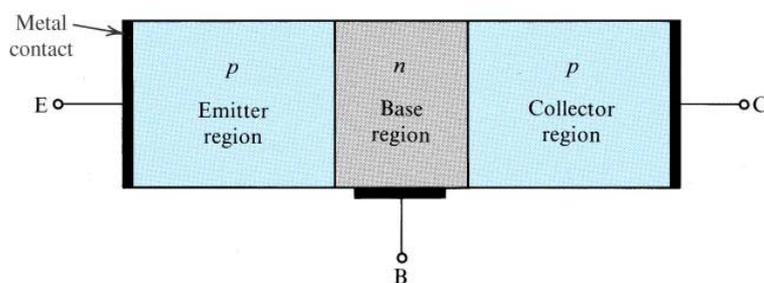


Figure 7.5: A simplified structure of the PNP transistor.

- Figure 7.5 depicts a simplified PNP transistor.
 - Emitter (E): heavily doped p-type region.

- Base (B): lightly doped n-type region.
- Collector (C): heavily doped p-type region.
- Two diodes connected in series with opposite directions.
 - * EBJ: Emitter-Base junction.
 - * CBJ: Collector-Base junction.
- Modes of operations
 - Cutoff
 - * EBJ (Reverse), CBJ (Reverse)
 - * $v_{EB} < 0, v_{BC} < 0$.
 - Active (refer to Figure 7.7)
 - * EBJ (Forward), CBJ (Reverse)
 - * $v_{EB} > 0, v_{BC} > 0$.
 - Reverse Active
 - * EBJ (Reverse), CBJ (Forward)
 - * $v_{EB} < 0, v_{BC} < 0$.
 - Saturation
 - * EBJ (Forward), CBJ (Forward)
 - * $v_{EB} > 0, v_{CB} > 0$.
- Figure 7.6 shows the voltage polarities and current flow in the PNP transistor biased in the active mode.

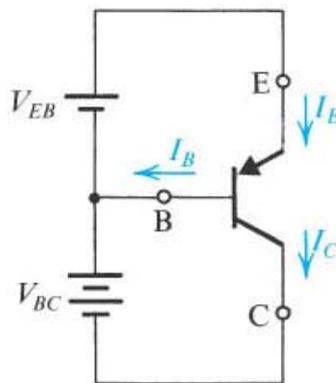


Figure 7.6: Voltage polarities and current flow in the PNP transistor biased in the active mode.

7.2 Operations of NPN Transistor

7.2.1 Active Mode

- Emitter-Base Junction

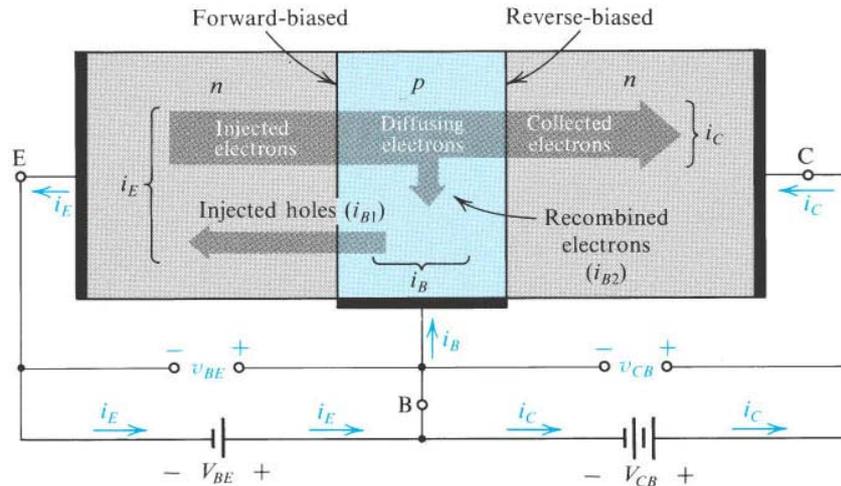


Figure 7.7: Current flow in an NPN transistor to operate in the active mode.

- Forward bias, $v_{BE} > 0$.
- Electrons in the emitter region are injected into the base causing a current i_{E1} .
- Holes in the base region are injected into the emitter causing a current i_{E2} .
- * Generally, $i_{E1} \gg i_{E2}$.

$$i_E(t) = i_{E1} + i_{E2} \quad (7.1)$$

- Base region

- Figure 7.8 depicts the concentration of minority carriers (electrons) in the base region.
- Tapered concentration causes the electrons to diffuse through the base region toward the collector.
 - * Some of the electrons may combine with the holes causing a concave shape of the profile.
 - * The recombination process is quite small due to lightly doped and thin base region.

$$n_p(0) = n_{p0} e^{v_{BE}/V_T} \quad (7.2)$$

- Diffusion current I_n (flowing from right to the left) is proportional to the slope of the concentration profile.
 - * A_E is the cross-sectional area of the base-emitter junction.
 - * D_n is the electron diffusivity in the base region.
 - * W is the effective width of the base.

$$I_n = A_E q D_n \frac{dn_p(x)}{dx} = -A_E q D_n \frac{n_p(0)}{W} \quad (7.3)$$

- Collector-Base Junction
 - Reverse bias, $v_{BC} > 0$.
 - The electrons near the collector side are swept into the collector region causing zero concentration at the collector side.

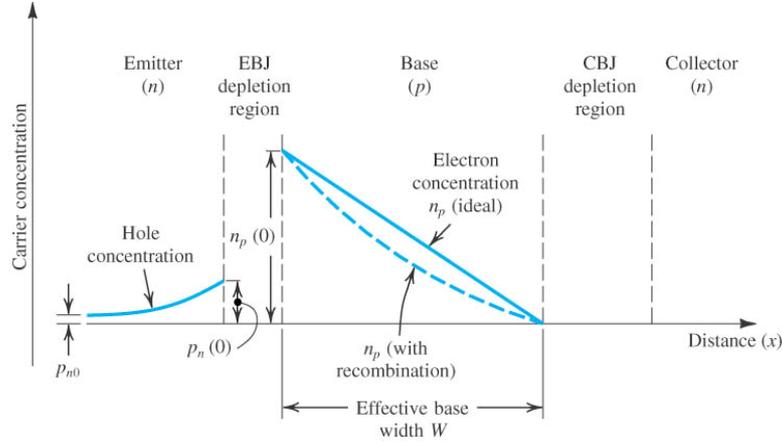


Figure 7.8: Profiles of minority carrier concentrations in the base and in the emitter of an NPN transistor.

- Collector current, i_C .
 - Most of the diffusing electrons will reach the collector region, i.e., $i_C = -I_n$.
 - * Only a very small percentage of electrons are recombined with the holes in the base region.
 - As long as $v_{CB} > 0$, i_C is independent of v_{CB} .
 - * The electrons that reach the collector side of the base region will be swept into the collector as collector current.

$$\begin{aligned}
 i_C &= -I_n \\
 &= A_E q D_n \frac{n_p(0)}{W} \\
 &= \frac{A_E q D_n n_{p0}}{W} e^{v_{BE}/V_T} \\
 &= \frac{A_E q D_n n_i^2}{W N_A} e^{v_{BE}/V_T} \\
 &= I_S e^{v_{BE}/V_T}
 \end{aligned} \tag{7.4}$$

- Saturation current (also known as scale current) $I_S = (A_E q D_n n_i^2) / (W N_A)$
 - * A strong function of temperature.
 - * Proportional to the cross-sectional area of the base-emitter junction.
 - * Inverse proportional to the base width W .

- Base current i_B

– i_B is composed of two currents.

- * The holes injected from the base region into the emitter region.

$$i_{B1} = \frac{A_E q D_p n_i^2}{N_D L_p} e^{v_{BE}/V_T} \quad (7.5)$$

- * The holes that have to be supplied by the external circuit due to the recombination.

- τ_b is the average time for a minority electron to recombine with a majority hole.

$$i_{B2} = \frac{1}{2} \frac{A_E q W n_i^2}{\tau_b N_A} e^{v_{BE}/V_T} \quad (7.6)$$

– Formulation of i_B in terms of i_C .

- * I_S is the saturation current of i_C (refer to Eq.(7.4))
- * $\beta = 1 / \left(\frac{D_p N_A W}{D_n N_D L_p} + \frac{1}{2} \frac{W^2}{D_n \tau_b} \right)$ is a constant (normally in the range 50 ~ 200) for a given transistor.
- * β is mainly influenced by (1) the width of the base region, and (2) the relative dopings of the base region and the emitter region $\frac{N_A}{N_D}$.
 - To achieve high β values, the base should be thin (W small) and lightly doped, and the emitter heavily doped.

$$\begin{aligned} i_B &= i_{B1} + i_{B2} \\ &= I_S \left(\frac{D_p N_A W}{D_n N_D L_p} + \frac{1}{2} \frac{W^2}{D_n \tau_b} \right) e^{v_{BE}/V_T} \\ &= \left(\frac{D_p N_A W}{D_n N_D L_p} + \frac{1}{2} \frac{W^2}{D_n \tau_b} \right) i_C \\ &= \frac{1}{\beta} \times i_C \end{aligned} \quad (7.7)$$

- Emitter current i_E

– From KCL, the i_E and i_C can be related as follows:

$$\begin{aligned} i_E &= i_B + i_C \\ &= \frac{1}{\beta} i_C + i_C \\ &= \frac{1 + \beta}{\beta} \times i_C \\ &= \frac{1}{\alpha} \times i_C \\ &= \frac{1}{\alpha} \times I_S e^{v_{BE}/V_T} \end{aligned} \quad (7.8)$$

- * $\alpha = \beta / (1 + \beta) \simeq 1$ is a constant for a given transistor.

- * Small change in α corresponds to large changes in β .
- Recapitulation
 - Configuration
 - * EBJ (Forward), CBJ (Reverse)
 - Relationship between i_C , i_B , and i_E .
 - * $i_C = \beta \times i_B$.
 - β (normally in the range 50~200) is a constant for a given transistor.
 - * $i_C = \alpha \times i_E$.
 - α ($\beta / (1 + \beta) \lesssim 1$) is a constant for a given transistor.
 - * i_B , i_C , and i_E are all controlled by v_{BE} .

$$\begin{aligned}
 i_C &= I_S e^{v_{BE}/V_T} \\
 i_B &= \frac{1}{\beta} I_S e^{v_{BE}/V_T} \\
 i_E &= \frac{1}{\alpha} I_S e^{v_{BE}/V_T}
 \end{aligned} \tag{7.9}$$

- Figure 7.9 depicts the large signal equivalent model of the NPN transistor.
 - * In Figure 7.9 (a), i_C behaves as a voltage (v_{BE}) controlled current source.

$$i_C + i_B = i_E = \frac{1}{\alpha} i_C \tag{7.10}$$

- * In Figure 7.9 (b), i_C behaves as a current (i_E) controlled current source.

$$\begin{aligned}
 i_C + i_B &= i_E \\
 \Rightarrow \alpha i_E + i_B &= i_E
 \end{aligned} \tag{7.11}$$

- * The diode D_E represents the forward base-emitter junction.

7.2.2 Reverse Active Mode

- The α and β in the reverse active mode are much lower than those in the forward active mode.
 - α_R is in the range of 0.01 to 0.5.
 - * In forward active mode, the collector virtually surrounds the emitter region.
 - Electrons injected into the thin base region are mostly captured by the collector.
 - * In reverse active mode, the emitter virtually surrounds the collector region.
 - Electrons injected into the thin base region are partly captured by the

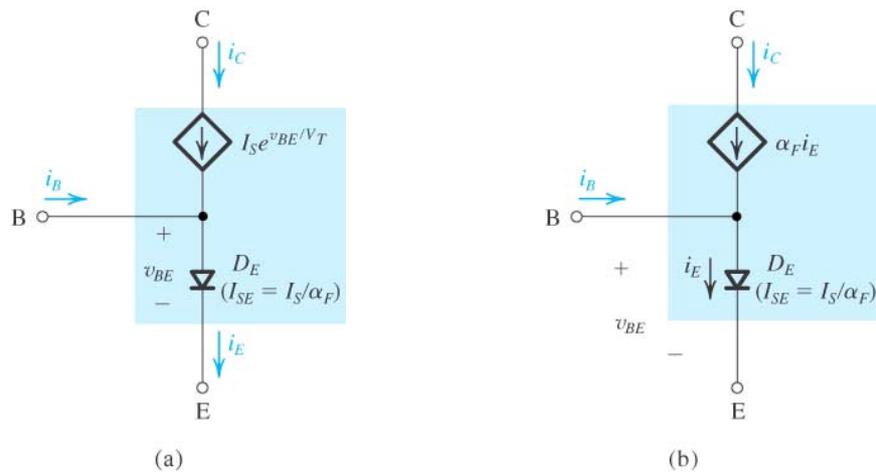


Figure 7.9: Large signal equivalent model of the NPN BJT operating in the forward active mode.

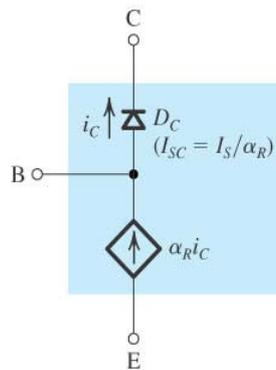


Figure 7.10: Large signal equivalent model of the NPN BJT operating in the reverse active mode.

collector.

- β_R is in the range of 0.01 to 1.
- CBJ has a much larger area than EBJ.
 - The diode D_C denotes the forward base-collector junction.
 - The diode D_C has larger scale current (I_{SC}) than D_E does.
 - * The diode D_C has lower voltage drop when forward biased.

7.2.3 Ebers-Moll (EM) Model

- A composite model that can be used to predict the operations of the BJT in all possible modes.
 - Combine Figure 7.9 (b) and Figure 7.10.
- α and β

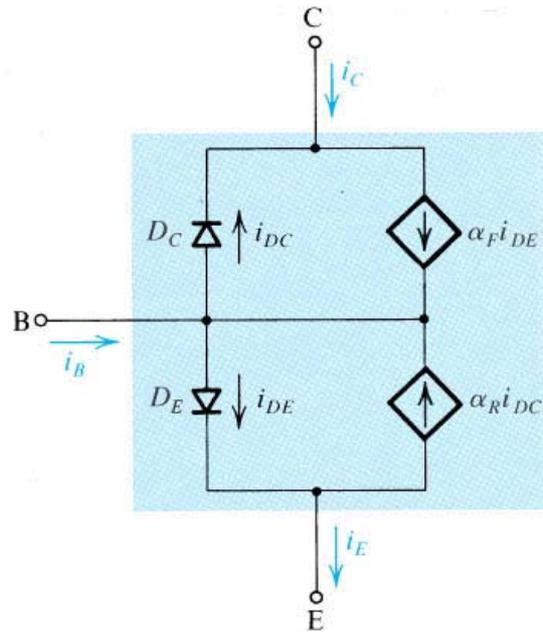


Figure 7.11: Ebers-Moll model of the NPN transistor.

- α_F and β_F denotes the parameters in forward active mode.
- α_R and β_R denotes the parameters in reverse active mode.
- Equivalent saturation current I_{SE} and I_{SC}
 - From Figure 7.9 (b) and Figure 7.10, I_{SE} and I_{SC} are the equivalent saturation currents at the EBJ and CBJ, respectively.

$$\begin{aligned}
 I_{SE} &= \frac{1}{\alpha_F} I_S \\
 I_{SC} &= \frac{1}{\alpha_R} I_S \\
 \Rightarrow \alpha_F I_{SE} &= \alpha_R I_{SC} = I_S
 \end{aligned} \tag{7.12}$$

- i_C , i_B , and i_E in the EM model

$$\begin{aligned}
 i_E &= i_{DE} - \alpha_R i_{DC} \\
 i_C &= -i_{DC} + \alpha_F i_{DE} \\
 i_B &= (1 - \alpha_F) i_{DE} + (1 - \alpha_R) i_{DC}
 \end{aligned} \tag{7.13}$$

- $i_{DE} = I_{SE} (e^{v_{BE}/V_T} - 1)$.
- $i_{DC} = I_{SC} (e^{v_{BC}/V_T} - 1)$.

- By Eq. (7.12),

$$\begin{aligned}
 i_E &= \frac{I_S}{\alpha_F}(e^{v_{BE}/V_T} - 1) - I_S(e^{v_{BC}/V_T} - 1) \\
 i_C &= I_S(e^{v_{BE}/V_T} - 1) - \frac{I_S}{\alpha_R}(e^{v_{BC}/V_T} - 1) \\
 i_B &= \frac{I_S}{\beta_F}(e^{v_{BE}/V_T} - 1) + \frac{I_S}{\beta_R}(e^{v_{BC}/V_T} - 1)
 \end{aligned} \tag{7.14}$$

- $\beta_F = \alpha_F / (1 - \alpha_F)$.
- $\beta_R = \alpha_R / (1 - \alpha_R)$.

7.2.4 Saturation Mode

- CBJ is in forward bias, i.e., $v_{BC} > 0.4V$.
 - CBJ has larger junction area than EBJ.
 - * CBJ has larger saturation current I_S and lower cut-in voltage than EBJ.
 - * In forward bias,
 - The voltage drop across CBJ is $0.4V$.
 - The voltage drop across EBJ is $0.7V$.
 - As v_{BC} is increased, i_C will be decreased and eventually reach zero.

$$i_C \simeq I_S e^{v_{BE}/V_T} - \frac{I_S}{\alpha_R} e^{v_{BC}/V_T} \tag{7.15}$$

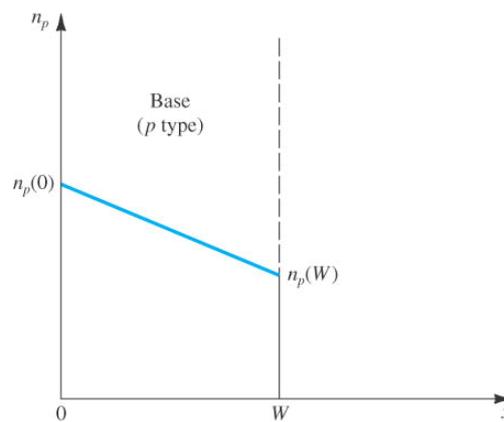


Figure 7.12: Concentration profile of the minority carriers in the base region of an NPN transistor.

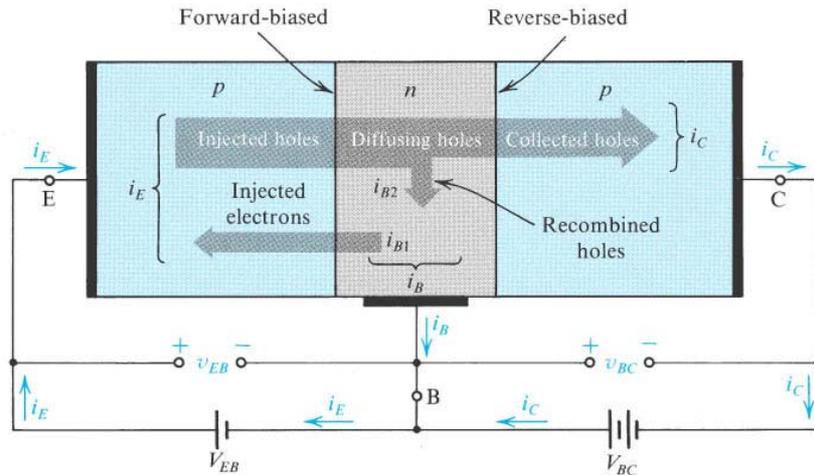


Figure 7.13: Current flow in a PNP transistor biased to operate in the active mode.

7.3 Operations of PNP Transistor

7.3.1 Active Mode

- Current in a PNP transistor is mainly conducted by holes.
- Emitter-Base Junction
 - Forward bias, $v_{EB} > 0$.
 - Holes in the emitter region are injected into the base causing a current i_{E1} .
 - Electrons in the base region are injected into the emitter region causing a current i_{E2} .

* Generally, $i_{E1} \gg i_{E2}$.

$$i_E(t) = i_{E1} + i_{E2} \quad (7.16)$$

- Base region
 - Tapered concentration causes the holes to diffuse through the base region toward the collector.
 - * Some of the holes may combine with the electrons.
 - * The recombination process is quite small due to lightly doped and thin base region.
- Collector-Base Junction
 - Reverse bias, $v_{BC} > 0$.
 - The holes near the collector side are swept into the collector region causing zero concentration at the collector side.
- Collector current, i_C .
 - Most of the diffusing holes will reach collector region.
 - * Only a very small percentage of holes are recombined with the electrons

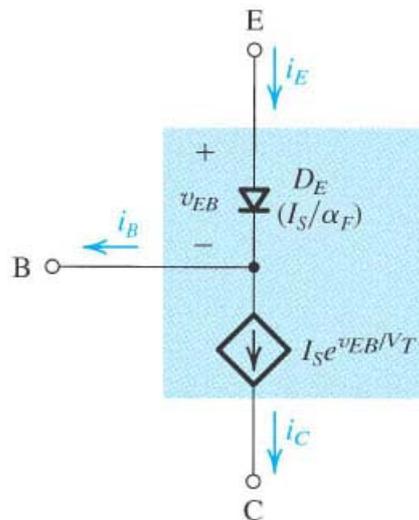


Figure 7.14: Large signal equivalent model of the PNP BJT operating in the forward active mode.

in the base region.

- As long as $v_{BC} > 0$, i_C is independent of v_{BC} .
 - * The holes that reach the collector side of the base region will be swept into the collector as collector current.
- Base current i_B
 - i_B is composed of two currents.
 - * The electrons injected from the base region into the emitter region.
 - * The electrons that have to be supplied by the external circuit due to the recombination.
- Emitter current i_E
 - From KCL, the i_E and i_C can be related as follows:

$$\begin{aligned}
 i_E &= i_B + i_C \\
 &= \frac{1}{\beta} i_C + i_C \\
 &= \frac{1 + \beta}{\beta} \times i_C \\
 &= \frac{1}{\alpha} \times i_C \\
 &= \frac{1}{\alpha} \times I_S e^{v_{EB}/V_T}
 \end{aligned} \tag{7.17}$$

- * $\alpha = \beta / (1 + \beta) \simeq 1$ is a constant for a given transistor.
- * Small change in α corresponds to large changes in β .
- Figure 7.14 depicts the large signal equivalent model of the PNP transistor.

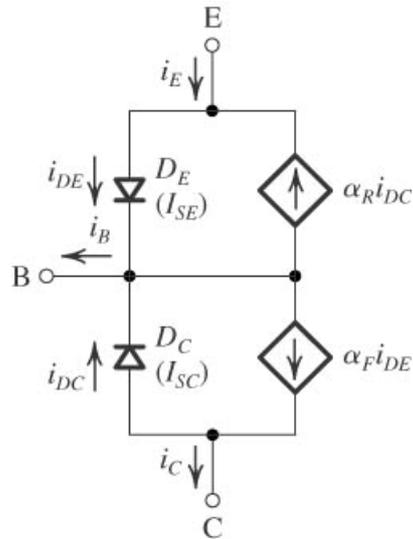


Figure 7.15: Ebers-Moll model of the PNP transistor.

- Figure 7.15 shows the EM model of the NPN transistor.

7.3.2 Reverse Active Mode

- Similar to NPN transistor.

7.3.3 Saturation Mode

- Similar to NPN transistor.

7.3.4 Summary of the i_C , i_B , i_E Relationships in Active Mode

- NPN transistor

$$\begin{aligned}
 i_c &= I_s e^{v_{BE}/V_T} \\
 i_B &= \frac{I_s}{\beta} e^{v_{BE}/V_T} \\
 i_E &= \frac{I_s}{\alpha} e^{v_{BE}/V_T}
 \end{aligned}
 \tag{7.18}$$

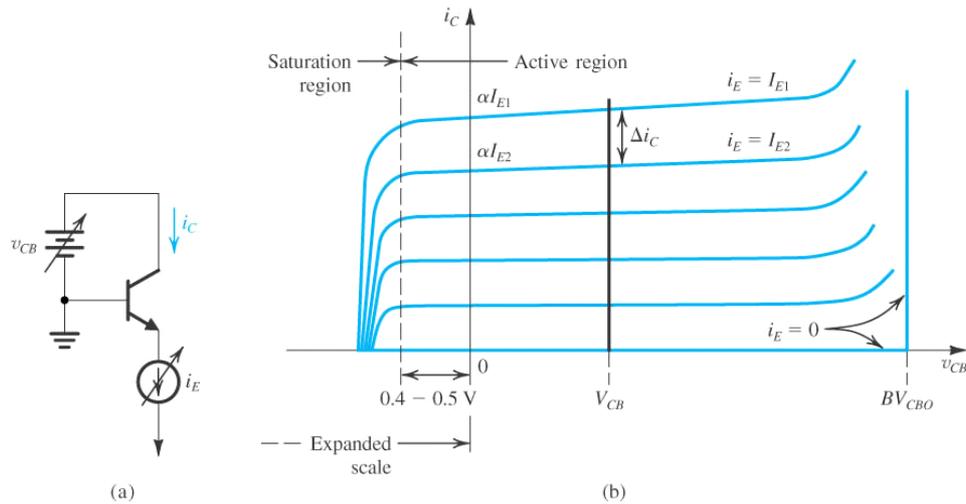


Figure 7.16: The $i_C - v_{CB}$ characteristics of an NPN transistor.

$$\begin{aligned}
 i_C &= \alpha i_E \\
 i_C &= \beta i_B \\
 i_B &= (1 - \alpha) i_E = \frac{i_E}{1 + \beta} \\
 i_E &= (1 + \beta) i_B
 \end{aligned} \tag{7.19}$$

- PNP transistor.
 - The v_{BE} in Eq. (7.18) is replaced by v_{EB} .

7.4 The $i - v$ Characteristics of NPN Transistor

7.4.1 Common Base ($i_C - v_{CB}$)

- Figure 7.16 depicts the i_C versus v_{CB} for various i_E , which is also known as the common-base characteristics.
 - Input port: emitter and base terminals.
 - * Input current i_E .
 - Output port: collector and base terminals.
 - * Output current i_C .
 - The base terminal serves as a common terminal to both input port and output port.
- Active Region ($v_{CB} \geq -0.4V$)
 - i_C depends slightly on v_{CB} and shows a small positive slope.

- i_C shows a rapid increase, known as breakdown phenomenon, for a relatively large value of v_{CB} .
- Each $i_C - v_{CB}$ curve intersects the vertical axis at a current level equal to αI_E .
 - * Total or large-signal α (common-base current gain)
 - $\alpha = i_C/i_E$, where i_C and i_E denote the total collector and emitter currents, respectively.
 - * Incremental or small-signal α
 - $\alpha = \Delta i_C/\Delta i_E$.
 - * Usually, the values of incremental and total α differs slightly.
- Saturation Region ($v_{CB} < -0.4V$)
 - CBJ is forward biased.
 - The EM model can be used to determine the v_{CB} at which i_C is zero.

7.4.2 Common Emitter ($i_C - v_{CE}$)

- Figure 7.17 depicts the i_C versus v_{CE} for various v_{BE} , which is also known as the common-emitter characteristics.
 - Input port: base and emitter terminals.
 - * Input current i_B .
 - Output port: collector and emitter terminals.
 - * Output current i_C .
 - The emitter terminal serves as a common terminal to both input port and output port.
- Active Region ($v_{CB} \geq -0.4V$)
 - i_C increases as the v_{CE} is increased, which is known as Early Effect.
 - * At a given v_{BE} , increasing v_{CE} increases the width of the depletion region of the CBJ.
 - * The effective base width W is decreased.
 - * As shown in Eq. (7.4), I_S is inversely proportional to the base width W .
 - When extrapolated, the characteristics line meet at point on the negative v_{CE} (normally in the range of 50V to 100V), $-V_A$.
 - * V_A is a constant for a given transistor.
- Large signal equivalent circuit model in active mode.
 - The linear dependency of i_C on v_{CE} can be formulized as follows:

$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A}\right) = I_C \left(1 + \frac{v_{CE}}{V_A}\right) \quad (7.20)$$

- The output resistance looking into the collector-emitter terminals.
 - * Inversely proportional to the collector current I_C without considering Early effect.

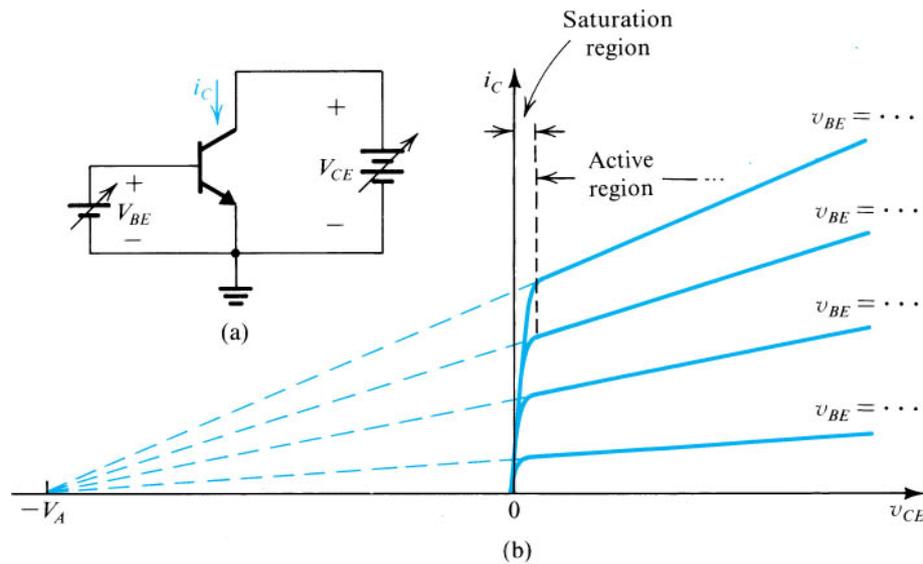


Figure 7.17: The $i_C - v_{CE}$ characteristics of the BJT.

- * Controlled by v_{BE} .

$$\Delta i_C = I_S e^{v_{BE}/V_T} \left(\frac{\Delta v_{CE}}{V_A} \right) \quad (7.21)$$

$$\Rightarrow r_o = \frac{\Delta v_{CE}}{\Delta i_C} = \frac{V_A}{I_C}$$

- Figure 7.18 depicts the large signal equivalent circuit model of an NPN BJT in the active mode and with the common emitter configuration.
 - * Figure 7.18 (a), voltage v_{BE} controls the collector current source.
 - * Figure 7.18 (b), the base current i_B controls the collector current source $\beta \times i_B$.
- Large signal or DC β
 - * The ratio of total current in the collector to the total current in the base, which represents the ideal current gain (where r_o is not present) of the common-emitter configuration.

$$\beta_{dc} = \left. \frac{i_C}{i_B} \right|_{v_{CE}=\text{constant}} \quad (7.22)$$

- * β is also known as the common-emitter current gain.
- Incremental or AC β
 - * Short-circuit common-emitter current gain.
 - * AC β and DC β differ approximately 10% to 20%.

$$\beta_{ac} = \left. \frac{\Delta i_C}{\Delta i_B} \right|_{v_{CE}=\text{constant}} \quad (7.23)$$

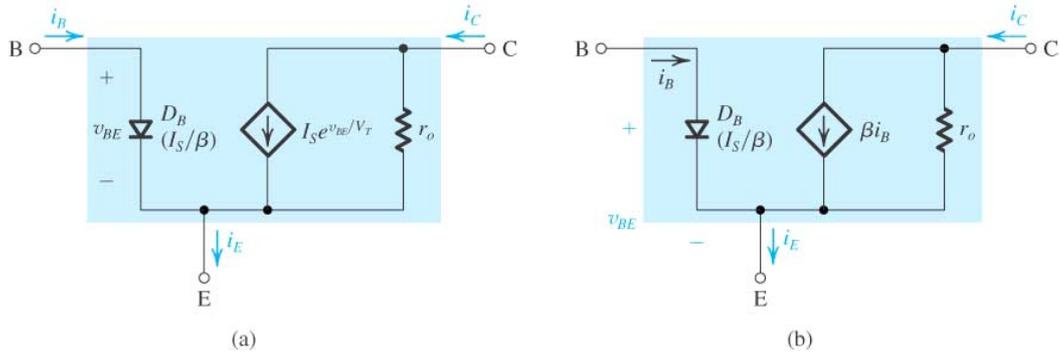


Figure 7.18: Large signal equivalent circuit model of an NPN BJT operating in the active mode and with common-emitter configuration.

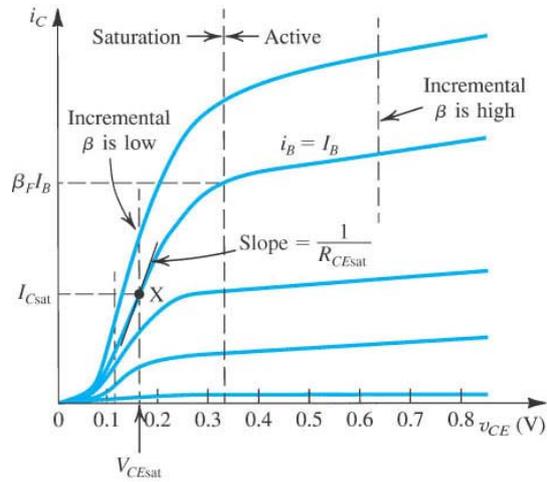


Figure 7.19: An expanded view of the common-emitter characteristic in the saturation region.

- Saturation Region ($v_{CB} < -0.4V$)
 - Figure 7.19 depicts an expanded view of the common-emitter characteristic in the saturation region.
 - Analytical expressions of $i_C - v_{CE}$ using EM model.
 - * $v_{BE} = v_{CE} + v_{CB}$.

$$\begin{aligned}
 i_C &\simeq I_S(e^{v_{BE}/V_T}) - \frac{I_S}{\alpha_R}(e^{v_{BC}/V_T}) \\
 I_B &\simeq \frac{I_S}{\beta_F}(e^{v_{BE}/V_T}) + \frac{I_S}{\beta_R}(e^{v_{BC}/V_T})
 \end{aligned} \tag{7.24}$$

$$i_C \simeq (\beta_F I_B) \left(\frac{e^{v_{CE}/V_T} - \frac{1}{\alpha_R}}{e^{v_{CE}/V_T} - \frac{\beta_F}{\beta_R}} \right) \tag{7.25}$$

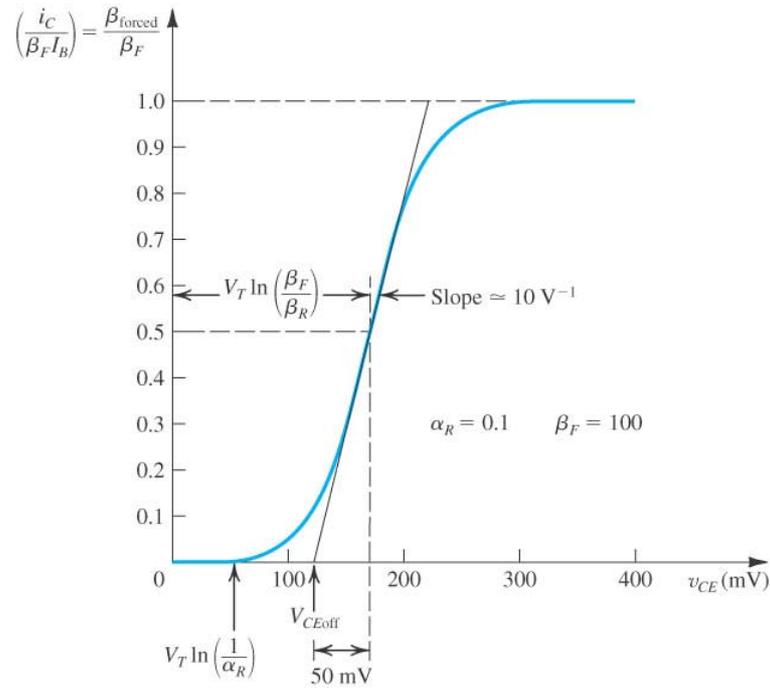


Figure 7.20: Plot of normalized i_C versus v_{CE} for an NPN transistor with $\beta_F = 100$ and $\alpha_R = 0.1$.

- Large signal equivalent circuit model in saturation mode.
 - The saturation transistor exhibits a low collector-to-emitter resistance R_{CEsat} .

$$R_{CEsat} = \left. \frac{\partial v_{CE}}{\partial i_C} \right|_{i_B=I_B, i_C=I_C} \simeq 1/10 \beta_F I_B \quad (7.26)$$

- At the collector side, the transistor is modeled as a resistance R_{CEsat} in series with a battery v_{CEoff} as shown in Figure 7.21 (c).
 - * V_{CEoff} is typically around $0.1V$.
 - * V_{CEsat} is typically around $0.1 \sim 0.3V$.

$$V_{CEsat} = V_{CEoff} + I_{Csat} R_{CEsat} \quad (7.27)$$

- For many applications, the even simpler model shown in Figure 7.21 is used.

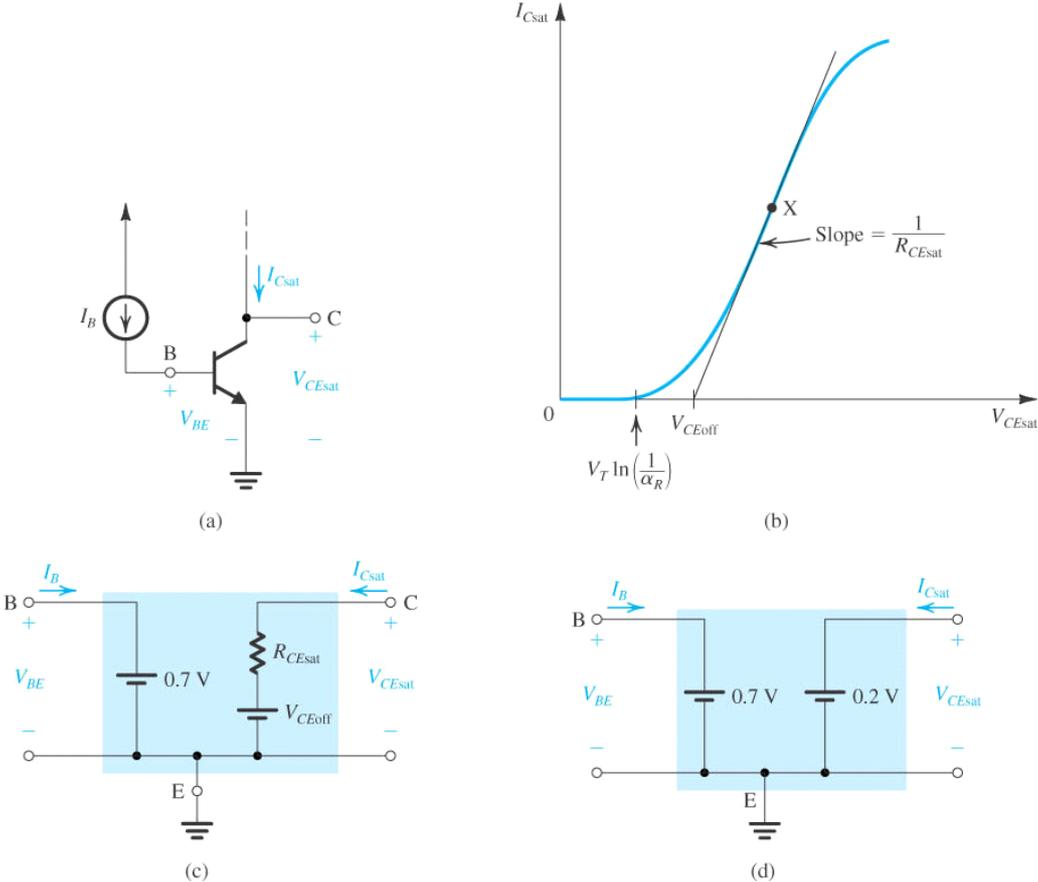


Figure 7.21: Equivalent circuit representation of the saturated transistor.